Expt. No. 03

Page No.

STAIR CASE WIRING

AIM :

To develop and test the staircase wiring using proteus.

APPARATUS REQUIRED :

Laptop with proteus software

Theory :

staircase wiring is a common multiple way switching (or) two way switching connection. It involves wiring for one light with two switches. In this setup is controlled by two switches located operator the load, from separate position above or below the staircase from inside or below the staircase from of two way led switch.

PROCEDURE :

* Drag the required componets from the process library.
* Connect the components as per circuit diagram.
* Run the simulation and check the lamp for different switching condition.

STAIRCASE WIRING

Circuit Diagram :

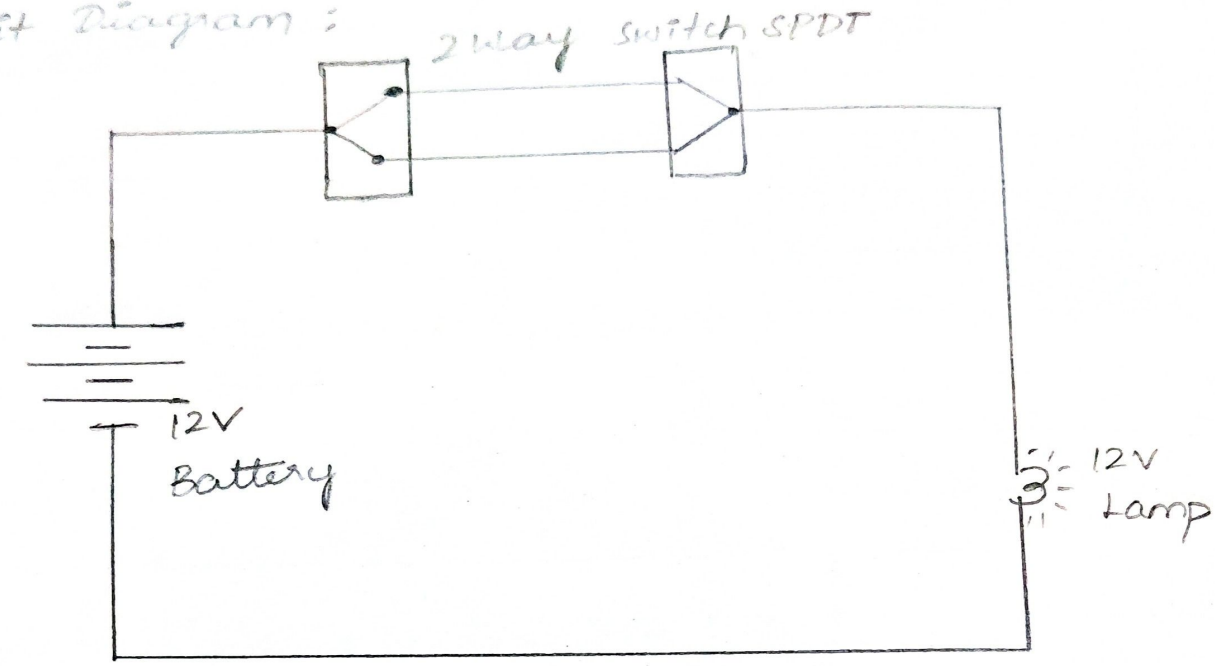

SPDT - Single pole double Throw switch.

S.NO	S1	S2	Lamp
1	ON	ON	ON
2	ON	OFF	OFF
3	OFF	ON	OFF
4	OFF	OFF	ON

Components	Protocols	Specification
AC Supply	Vsine	Amplitude 230V
Two-way switch	SPDT	Frequency 50Hz
Lamp	Animated	230V

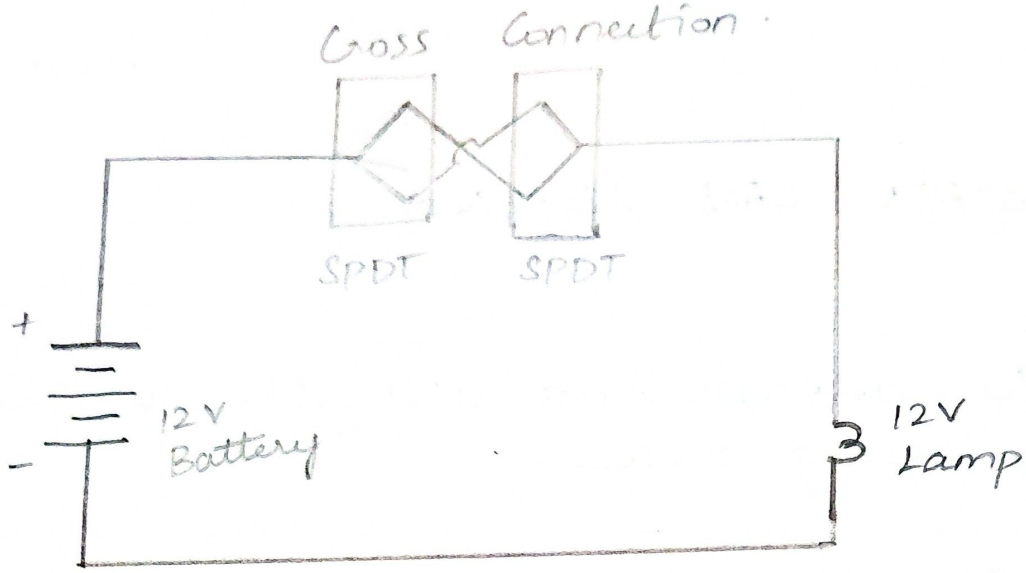

Mode	S1	S2	Lamp
1	ON	ON	OFF
2	ON	OFF	ON
3	OFF	ON	ON
4	OFF	OFF	OFF

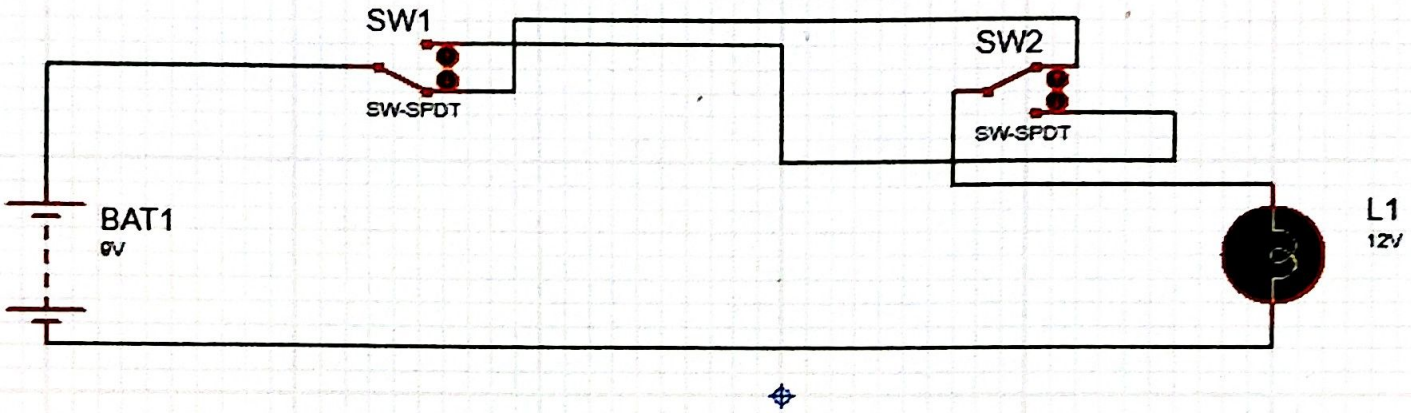
SW1
SW-SPDT
SW2
SW-SPDT
BAT1
9V
L1
12V

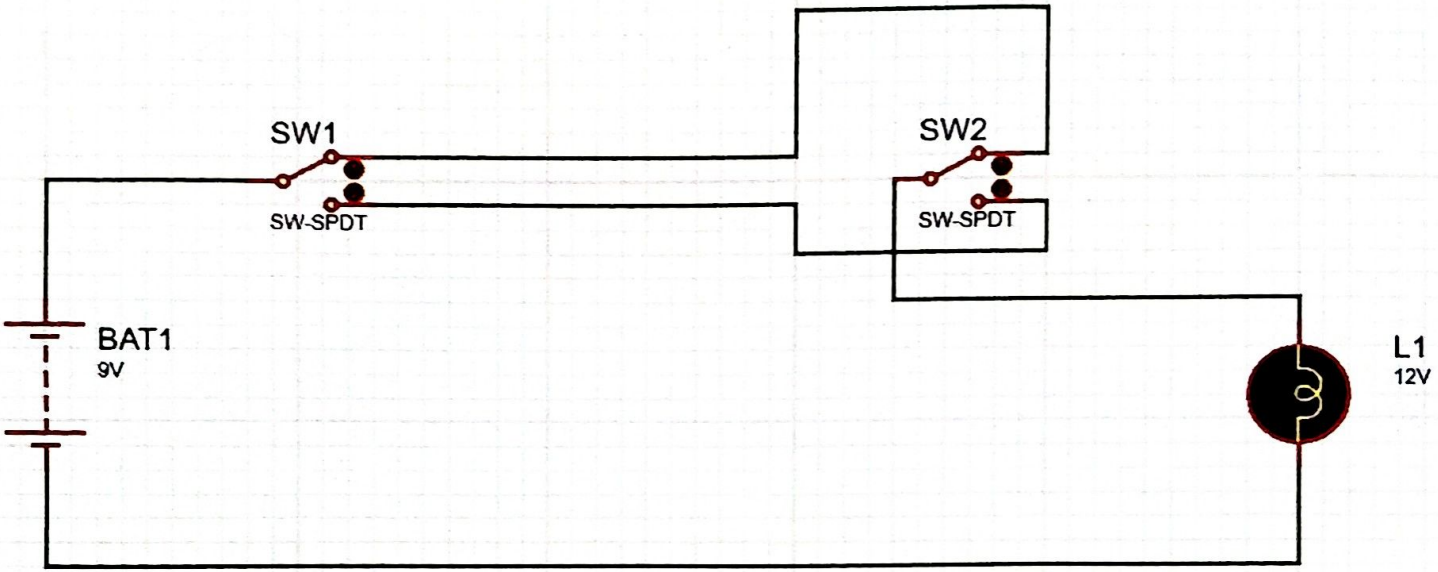
SW1
SW-SPDT
SW2
SW-SPDT
BAT1
9V
L1
12V

Expt. No.

Page No.

100

11/03/20

RESULT :

Thus the staircase using Connection were developed and tested successfully.